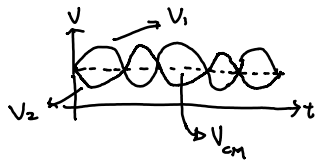


Bipolar Differential Pairs

Differential Signals

- Vary by equal and opposite amounts
- Same average DC value



V_{cm} : common-mode level

$$V_1(t) = V_o \sin \omega t + V_{cm}$$

$$V_2(t) = -V_o \sin \omega t + V_{cm}$$


Notice that:

$$V_1 - V_2 = 2V_o \sin \omega t$$


$$V_{sig} = \frac{V_1 - V_2}{2} = V_o \sin \omega t$$

The immediate question is how do we generate differential signals???

The Differential Pair

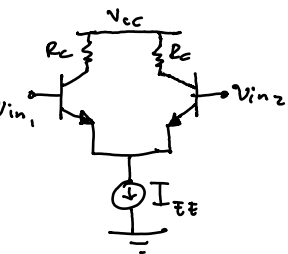


BJT Differential Pair

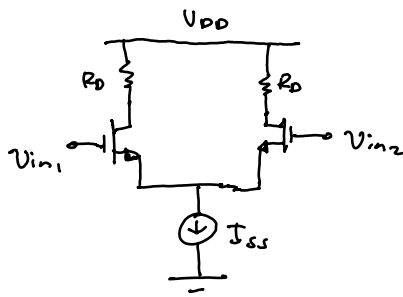

MOS Differential Pair

Review of Common Emitter Configuration

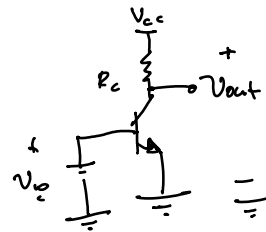


What is V_{out} ???

$$I_c = I_s \exp\left(\frac{V_b}{V_T}\right)$$

$$V_{out} = V_{DD} - I_c R_c$$

Consider the circuit

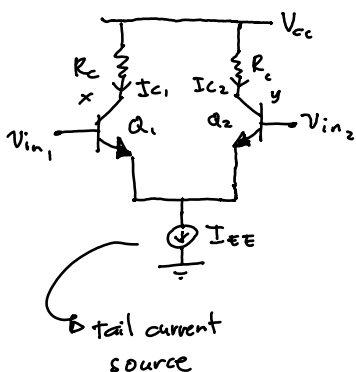

Case 1: The bases of Q_1 and Q_2 are shorted and connected to a battery.

$$V_{in1} = V_{in2} = V_{CM, in}$$

$$\text{KCL: } I_{C1} + I_{C2} = I_{EE}, \text{ if } I_{C1} = I_{C2}, \text{ then } I_{C1} = I_{C2} = \frac{1}{2} I_{EE}$$

$$\text{Voltage Drop across } R_c = \frac{1}{2} I_{EE} R_c$$


$$V_x = V_{cc} - \frac{1}{2} I_{EE} R_c = V_y$$

$$\text{If } V_{in1} - V_{in2} = 0, \text{ then } V_x - V_y = 0$$

Differential Input Voltage
Differential Output Voltage

∴ If there is perturbation in V_{in1} and V_{in2} , the circuit is oblivious to that change. the differential pair rejects changes in input CM level.

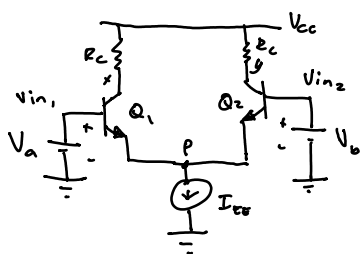Case 2: V_{in1} and V_{in2} are not the same ($V_{in1} - V_{in2} \neq 0$)



Guess: Q_1 is on and has some current

Question: Is Q_2 ON???

$$\text{Assume } V_{BE1} = 800 \text{ mV}, V_a = 2.5 \text{ V}, V_b = 1.5 \text{ V}$$

$$\text{thus, } V_p = V_a - V_{BE1} = 1.7 \text{ V}$$


$$Q_2 \text{ is off since } V_{s12} > V_{D12}$$

∴ All of I_{EE} flows through Q_1

In response to an imbalance at the input, there came an imbalance to the output.

$$V_x = V_{cc} - R_c I_{EE}, \quad V_y = V_{cc} \text{ (since } I_{C2} = 0)$$

First Input-Output Characteristic

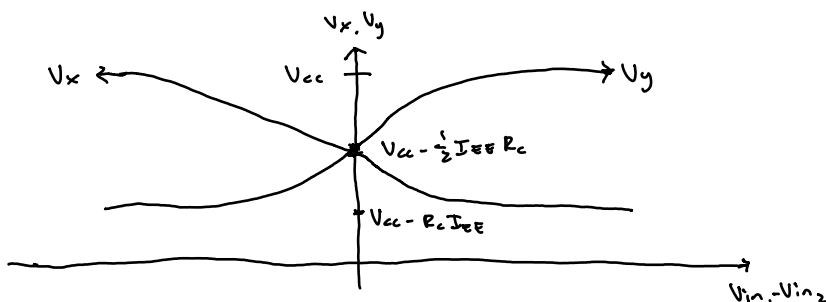


• Characteristic Plot is similar to the plot of differential signals.


• This is just an "intuitive" approach to the differential pair.

Large and Small Signal Analysis of Bipolar Differential Pair

Large-Signal Analysis

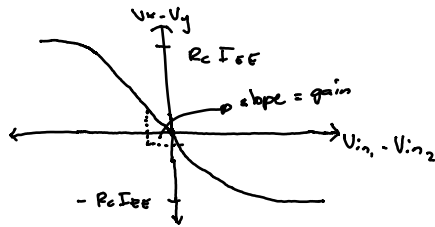


The slope is the gain of an amplifier

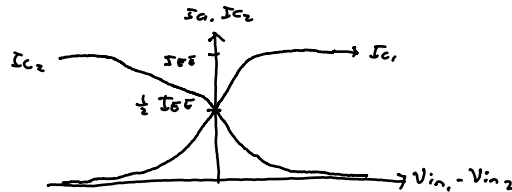

We have obtained graphs for $V_x - V_y$ and I_{C1}, I_{C2} as a function of $V_{in1} - V_{in2}$

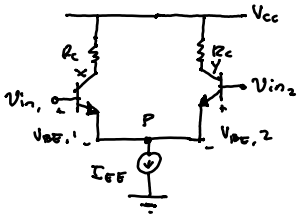Objective: Derive equations for I_{C1}, I_{C2}, V_x, V_y , and $V_x - V_y$ as a function of $V_{in1} - V_{in2}$.



Remember that:

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

① If $V_{in1} = V_{in2}$, the current splits equally.

② If $V_{in1} - V_{in2}$ is positive enough, I_{C1} and I_{C2} differs.

Notice that:

$$V_{in1} - V_{BE,1} = V_{in2} - V_{BE,2}$$

$$V_{in1} - V_{in2} = V_{BE,1} - V_{BE,2}$$

$$= V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right)$$

$$= V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right)$$

* These transistors are identical ($I_{S1} = I_{S2}$)

$$I_{C1} + I_{C2} = I_{EE}$$

$$I_{C1} = I_{C2} \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)$$

$$I_{C1} + I_{C2} \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right) = I_{EE}$$

$$I_{C2} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}$$

where $V_T = 26 \text{ mV}$ @ 300°K

The plot is similar to the inverted hyperbolic tangent.

similarly,

$$I_{C1} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in2} - V_{in1}}{V_T}\right)}$$

$$V_x = V_{CC} - R_C I_{C1}$$

$$V_y = V_{CC} - R_C I_{C2}$$


$$V_x - V_y = R_C I_{C2} - R_C I_{C1}$$

$$\text{or } V_x - V_y = -R_C I_{EE} \tanh\left(\frac{V_{in1} - V_{in2}}{2V_T}\right)$$

$$R_C I_{EE} \left[\frac{1}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)} - \frac{1}{1 + \exp\left(\frac{V_{in2} - V_{in1}}{V_T}\right)} \right]$$

If $\frac{V_{in1} - V_{in2}}{V_T} \ll 1$, then by the Taylor expansion, $\tanh\left(\frac{V_{in1} - V_{in2}}{2V_T}\right) \approx \frac{V_{in1} - V_{in2}}{2V_T}$ $\Rightarrow V_x - V_y \approx -R_C I_{EE} \left(\frac{V_{in1} - V_{in2}}{2V_T}\right)$, slope = $-\frac{R_C I_{EE}}{2V_T}$

Small-Signal Analysis

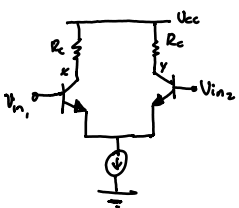

If V_{in1} increases by ΔV , V_x decreases by ΔV .

then,

$$V_x - V_y = -R_C I_{EE} \tanh\left(\frac{2\Delta V}{2V_T}\right)$$

$$\approx -\frac{R_C I_{EE}}{2V_T} (2\Delta V)$$

If $-\frac{R_C I_{EE}}{2V_T} \gg 1$, amplification happens

$$V_x = V_{CC} - R_C I_{C1}$$

$$V_y = V_{CC} - R_C I_{C2}$$

$$V_x - V_y = -R_C [I_{C1} - I_{C2}] = -R_C I_{EE} \left(\frac{\Delta V}{V_T}\right)$$

$$I_{C1} - I_{C2} = I_{EE} \frac{\Delta V}{V_T}, \text{ and } I_{C1} + I_{C2} = I_{EE}$$

$$\text{thus, } \frac{I_{C1} - I_{C2}}{I_{C1} + I_{C2}} = \frac{I_{EE} \frac{\Delta V}{V_T}}{I_{EE}}$$

$$2I_{C1} = I_{EE} \left(1 + \frac{\Delta V}{V_T}\right)$$


$$I_{C1} = \frac{1}{2} I_{EE} \left(1 + \frac{\Delta V}{V_T}\right)$$

$$\Delta I_{C1} = \frac{I_{EE}}{2V_T} \Delta V$$

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}}$$

$$\Delta I_C = g_m \Delta V_{BE}$$

Basic Concepts:

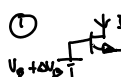

$$g_m = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{I_C}{V_T}$$



$$\Delta V_{BE} = \frac{\left(\frac{I_{EE}}{2V_T} \Delta V\right)}{\frac{I_{EE}}{2V_T}} = \Delta V$$

Lemma: If V_{in1} and V_{in2} change by equal and opposite amounts, then the tail node voltage does not change. (if the change is small)


\therefore If the voltage in V_{BE1} increases by ΔV , then V_{BE2} changes by the same amount. Thus, V_P remains the same.

Small-Signal Behavior

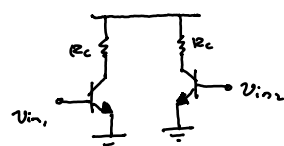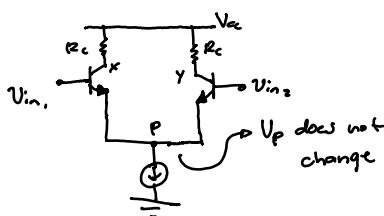V_P is considered virtual ground since it does not change with time.



Actual small-signal model

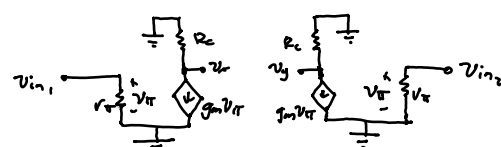

$$V_x = -g_m R_C V_{in1}$$


$$V_x - V_y = -g_m R_C (V_{in1} - V_{in2})$$

$$V_y = -g_m R_C V_{in2}$$

$$A_v = \frac{V_x - V_y}{V_{in1} - V_{in2}} = -g_m R_C$$

More on Bipolar Differential Pairs

Additional Examples:

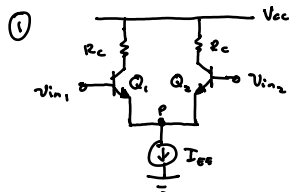

Let $I_{EE} = 1 \text{ mA}$
 $R_C = 1 \text{ k}\Omega$
 $I_S = 2 \times 10^{-15} \text{ A}$

Questions:

- Determine the bias conditions
- Construct the I/O characteristic
- Obtain the voltage gain.

Solution:


- Bias conditions:

$$I_{C1} = I_{C2} = \frac{1}{2} I_{EE}$$

$$\text{since } I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right),$$


$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

$$V_{BE,1} = V_{BE,2} = 862 \text{ mV}$$

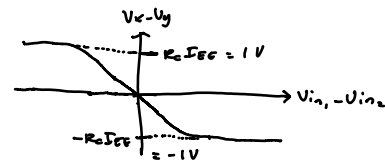

• small-signal gain = $-g_m R_C$

$$= \frac{-R_C I_{EE}}{2V_T} = -19.2$$

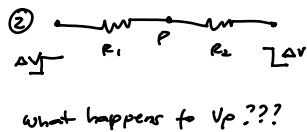

Answer


Let $R_1 = R_2 = R$

$$I = \frac{\Delta V}{2R} = \frac{\Delta V}{R}$$

Voltage Drop across R_1

$$\Rightarrow \frac{\Delta V}{R} R = \Delta V$$

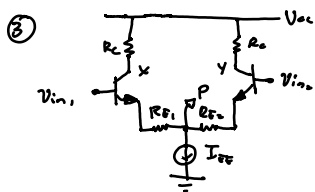If we increase V_{in} by ΔV ,
 the voltage drop across R_1
 increases by ΔV . $\Rightarrow V_P$ is constant



* Bipolar Differential Pair with Emitter Degeneration

Let $R_{E1} = R_{E2} = R_E$

• Since V_P does not change with time, we can draw two separate circuits



$$\frac{-R_C}{\frac{1}{g_m} + R_E} = \frac{-g_m R_C}{1 + g_m R_E} \Rightarrow \text{less slope}$$

gain decreases around $V_{in1} - V_{in2} = 0$

\therefore Emitter degeneration improves linearity

Thus,
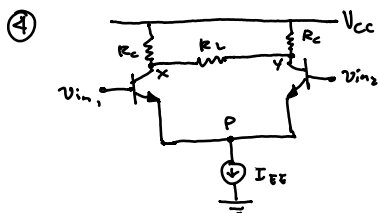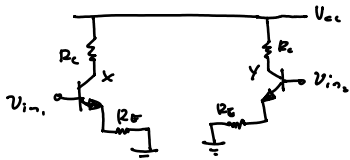
$$\frac{V_X - V_Y}{V_{in1} - V_{in2}} = \frac{-R_C}{\frac{1}{g_m} + R_E}$$





If V_{in1} and V_{in2} changes differentially,

V_X and V_Y also changes differentially.

* the circuit is grounded along the point of symmetry.

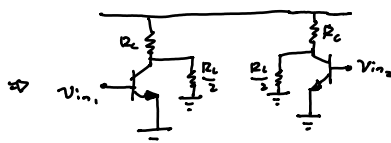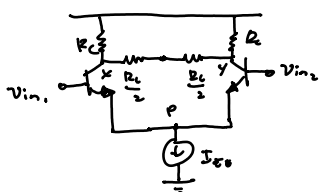
We can replace R_C with 2 series resistors



$$\therefore A_v = -g_m \left(R_C \parallel \frac{R_L}{2} \right)$$

We decomposed R_L to find the point of symmetry.

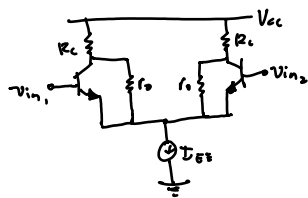
\therefore If early effect is considered,



$$A_v = -g_m (R_C \parallel r_o)$$

as far as small signals are concerned.

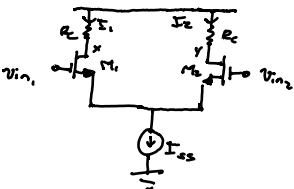Large Signal Analysis of MOS Differential Pair



cases:

① V_{in1} and V_{in2} are shorted. They are connected to V_{cm} .

Thus, $I_1 = I_2 = \frac{1}{2} I_{SS}$.

$$V_x \approx V_y = V_{DD} - \frac{R_D I_{SS}}{2}$$

If $V_{in1} = V_{in2}$, the differential pair is in equilibrium.


$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$V_{GS} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$


where

$$\sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

is the equilibrium overdrive voltage

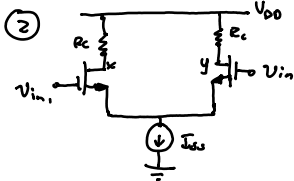

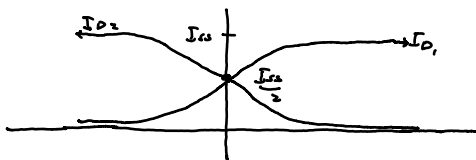② If V_{in1} and V_{in2} are different, the characteristic plot looks like this:




* If V_{in1} is much greater than V_{in2} ,

All of I_{SS} flows through M_1 , and

M_2 is off.

• Condition: MOS should be in saturation

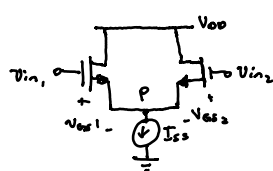Question: What is the minimum value of $V_{in1} - V_{in2}$ at which one transistor turns off???



If M_2 is off, then

$$V_{GS2} = V_{TH}$$

If all of I_{SS} flows through M_1 ,


$$V_{GS1} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

$$\text{Thus, } V_P = V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

$$= \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

• Large Signal Analysis

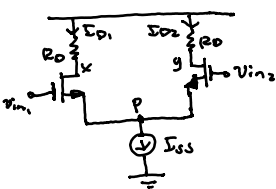

By KVL,

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

Assume that both of the transistors are on.

$$V_{in1} - V_{in2} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} - \left(\sqrt{\frac{2 I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH} \right)$$

similarly,

$$V_x = V_{DD} - R_D I_{D1}$$

$$V_y = V_{DD} - R_D I_{D2}$$

$$V_x - V_y = -R_D (I_{D1} - I_{D2})$$

$$I_{D1} + I_{D2} = I_{SS}$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}} + \frac{2 I_{D2}}{\mu_n C_{ox} \frac{W}{L}}$$

$$- \frac{2 \sqrt{4 I_{D1} I_{D2}}}{\mu_n C_{ox} \frac{W}{L}}$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} = \frac{-9 \sqrt{I_{D1} (I_{SS} - I_{D1})}}{\mu_n C_{ox} \frac{W}{L}}$$

If we solve the equation:

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

Observations:

① $I_{D1} - I_{D2} = 0$ if $V_{in1} = V_{in2}$

* If $V_{in1} - V_{in2} > \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}$, one transistor

turns off.

② If $V_{in1} - V_{in2}$ exceeds a certain amount, one transistor turns off. The equation is no longer valid.

Question:

• What happens if I_{SS} is doubled?


∴ slope changes to

$$- \sqrt{2} R_D \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$

∴ Increased linearity around the origin.

• What happens if W is doubled?

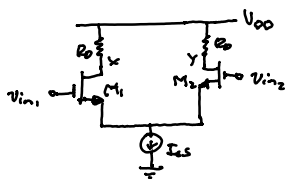∴ circuit becomes sharper but less linear.




$$V_x - V_y = -R_D (I_{D1} - I_{D2})$$

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

this equation is valid iff:

$$|V_{in1} - V_{in2}| \leq \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

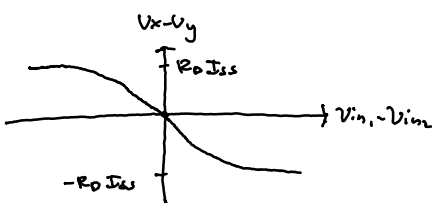

$$\text{If } V_{in1} - V_{in2} \ll \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$\Rightarrow V_x - V_y = -R_D \mu_n C_{ox} \frac{W}{L} \sqrt{\frac{4 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$


$$V_x - V_y \approx -R_D \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (V_{in1} - V_{in2})$$

$$\text{slope} = - \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D$$

Small Signal Analysis of MOS Differential Pair

• Small-signal Behavior of MOS Differential Pair


Few Points

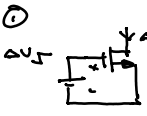①  $\Delta I \approx \frac{\Delta I}{\Delta V} = g_m$
 $\Delta I = g_m \Delta V$

V_{GS} changes by

$$\frac{\sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \Delta V}{\sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}} = \Delta V$$

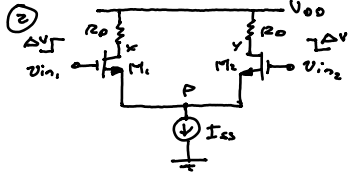thus, V_P is constant and is equivalent to an AC ground.



$$V_x - V_y = -R_0 \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (2 \Delta V)$$

$$= -R_0 (I_{D1} - I_{D2})$$


$$\therefore I_{D1} - I_{D2} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (2 \Delta V)$$

$$+ I_{D1} + I_{D2} = I_{SS}$$

$$2 I_{D1} = I_{SS} + \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (2 \Delta V)$$

$$I_{D1} = \frac{I_{SS}}{2} + \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} (\Delta V)$$

• Small-signal equivalent

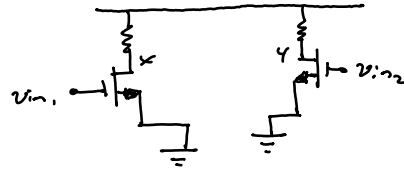


$$\frac{V_x}{V_{in1}} = -g_m R_0, \quad \frac{V_y}{V_{in2}} = -g_m R_0$$


thus,

$$\frac{V_x - V_y}{V_{in1} - V_{in2}} = -g_m R_0$$

• Examples:

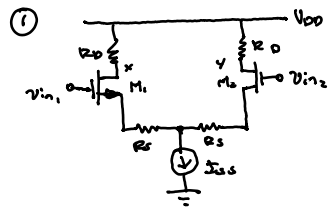
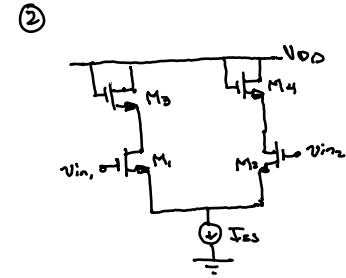
$$\frac{V_x}{V_{in1}} = -\frac{R_0}{\frac{1}{g_m} + R_s} \quad \text{or} \quad \frac{V_x - V_y}{V_{in1} - V_{in2}} = \frac{-R_0}{\frac{1}{g_m} + R_s}$$




Note that

A diode connected device acts as a resistor

$$\text{diode connected MOSFET} \quad R_{in} = \frac{1}{g_m}$$

Note: neglecting channel-length modulation

$$A_v = \frac{-g_{m1}}{g_{m2}}$$

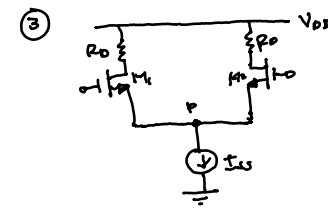

What if $\omega \rightarrow 2\omega$?

$$-g_m \rightarrow \sqrt{2} g_m$$

$$A_v \rightarrow \sqrt{2} A_v$$

④ What happens if $I_{SS} \rightarrow 2I_{SS}$ and $\omega \rightarrow 2\omega$???


$$g_m \rightarrow 2g_m$$

$$A_v \rightarrow 2A_v$$


⑤ What happens if temperature rises???

$$g_m \downarrow \text{ since } \mu_n \downarrow \Rightarrow |A_v| \downarrow$$

• P-type Differential Pairs

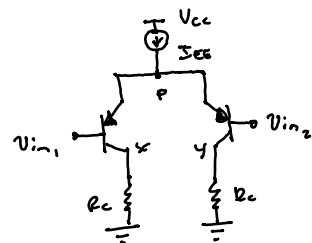

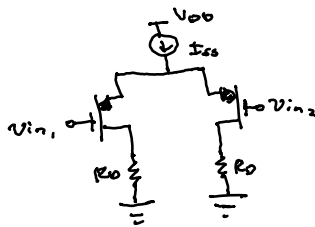
• the calculations are similar to the NPN BJT



• All calculations are similar to NMOS

High - Gain Differential Pairs

- We need a load that doesn't satisfy Ohm's law.

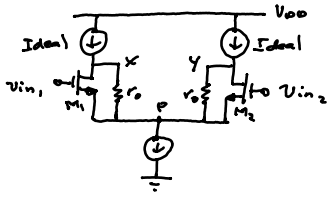


Approach I: v_p is constant

$\Rightarrow P$ is AC GND.



$$\therefore \Delta v = -g_m r_o$$

the circuit is equivalent to

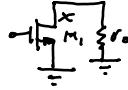

where $A_0 = -g_m r_o$


- Differential Pair with Cascode Load

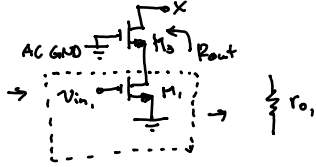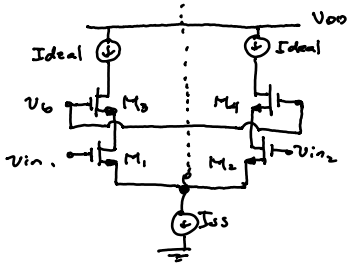

$$\rightarrow R_{out} = (1 + g_{m3} r_{o3}) r_{o1} + r_{o3}$$

$$\approx g_{m3} r_{o3} r_{o1}$$
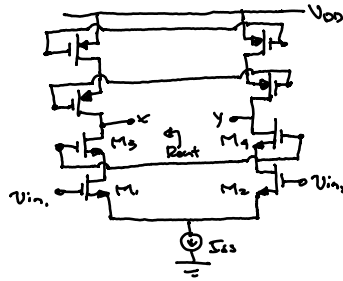
$$\therefore A_v = -g_{m_1} r_{o_1} g_{m_3} r_{o_3}$$




$$G_m = g_m,$$

$$Z_{out} = [(1 + g_{m3} r_{o3}) r_{o1} + r_{o3}] \parallel$$

$$[(1+g_{n-1}r_{n-1})r_n + r_m]$$


$$\therefore A_v = -G_m R_{out}$$

- Differential Pair with Active load

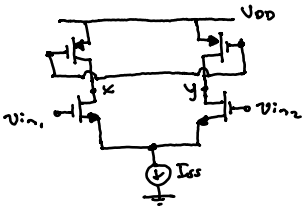

- What if I want to connect x and y to a single-ended input stage??
 - If x is connected and y is left out then A_v is halved.


- Consider

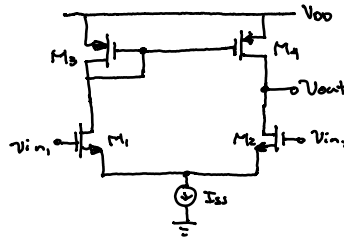

If V_{in1} increases by ΔV and V_{in2} decreases by the same amount, then $I_{C1} \uparrow$ and $I_{C2} \downarrow$.

$\therefore V_{out}$ increases.

- Going back to current mirrors,

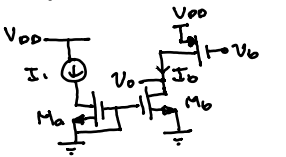

NMOS current mirror

If $I_1 \rightarrow I_1 + \Delta I_1$
 V_0 decreases.


why?

$$v_o = v_{od} - i_o(z) \text{ for some impedance}$$

z.

$$I_D \uparrow = v_o \downarrow$$

Conversely, for a PMOS current mirror,

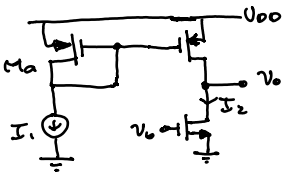


If $I_1 \rightarrow I_1 + \Delta I_1$,
 v_0 increases.

why?

$$V_0 = \mathcal{I}_0(z) \text{ for some impedance } z.$$

thus, $I_0 \tau = V_0 \tau$.

Going back,

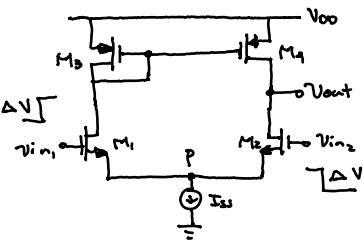


- Boat wants to go up if V_1 increases.
- Boat wants to go up if V_2 decreases

v_0 wants to go up (intuitively)

Small Signal Behavior of Differential Pair with Active Load

Consider the circuit

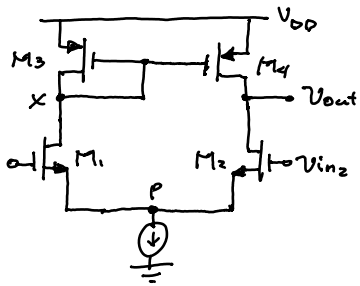

- this circuit has two signal paths
- * Path from M1
- * Path from M2

Questions:

- ① How much is the voltage change at X?
- ② How much is the voltage change at the output?

Answers:


- ① the equivalent impedance of R_o is $\frac{1}{g_m} \parallel r_o$
thus, $\Delta V_x = \Delta I \left(\frac{1}{g_m} \parallel r_o \right) \approx \frac{\Delta I}{g_m}$

- ② Resistance seen by the output node is $r_{o,n} \parallel r_{o,p}$, thus,
 $\Delta V_{out} = \Delta I (r_{o,n} \parallel r_{o,p})$

→ Change in $V_x < \text{Change in } V_{out}$

$$\dot{A}_v = \frac{V_{out}}{V_{in1} - V_{in2}}$$

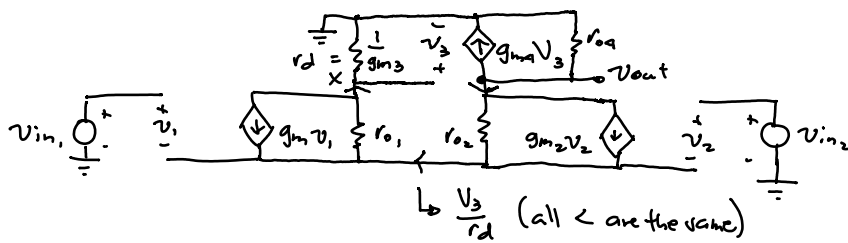- Small-signal Voltage Gain
- * P is not AC GND!!!



KCL at the output:

$$\frac{V_3}{r_d} + \frac{V_{out}}{r_{o4}} + g_{m4}V_3 = 0$$

$$V_3 = \frac{-V_{out}}{r_{o4}(2g_{mp})} = \frac{-V_{out}}{r_{o,p}(2g_{mp})}$$

KCL at X:

$$g_m V_1 + \frac{V_3 - V_P}{r_{o1}} + \frac{V_3}{r_d} = 0$$

KCL at output:

$$g_m V_2 + \frac{V_{out} - V_P}{r_{o2}} - \frac{V_3}{r_d} = 0$$

$$(-) \rightarrow g_{m,n}(V_1 - V_2) + \frac{V_3 - V_{out}}{r_{o,n}} + \frac{2V_3}{r_d} = 0$$

$$V_1 - V_2 = V_{in1} - V_{in2}, \text{ thus } g_{m,n}(V_{in1} - V_{in2}) + \frac{V_3 - V_{out}}{r_{o,n}} + \frac{2V_3}{r_d} = 0$$

$$\text{since } V_3 = \frac{-V_{out}}{r_{o,p}(2g_{mp})}, \quad g_{m,n}(V_{in1} - V_{in2}) + \frac{-V_{out}}{2g_{mp}r_{o,p}r_{o,n}} - \frac{V_{out}}{r_{o,n}} - \frac{2V_{out}}{2g_{mp}r_{o,p}r_d} = 0$$

$$g_{m,n}(V_{in1} - V_{in2}) = V_{out} \left[\frac{1}{2g_{mp}r_{o,p}r_{o,n}} + \frac{1}{r_{o,n}} + \frac{1}{r_{o,p}} \right]$$

↳ negligible ≈ 0 .

$$\text{Thus, } \frac{V_{out}}{V_{in1} - V_{in2}} = -g_{m,n}(r_{o,n} \parallel r_{o,p}) \rightarrow \text{same as the gain of fully differential output!!!}$$